

BOOLEAN METHODS

© *Giovanni De Micheli*

Stanford University

Boolean methods

© GDM

- Exploit Boolean properties.
 - *Don't care* conditions.
- Minimization of the local functions.
- Slower algorithms, better quality results.


External *don't care* conditions

© GDM

- *Controllability don't care* set CDC_{in} :
 - Input patterns never produced by the environment at the network's input.
- *Observability don't care* set ODC_{out} :
 - Input patterns representing conditions when an output is not observed by the environment.
 - Relative to each output.
 - Vector notation used: **ODC**_{out}.

Example

© GDM

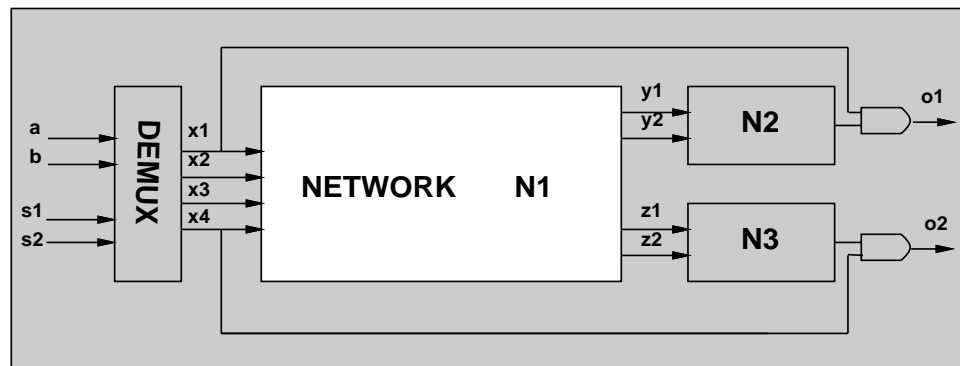

- Inputs driven by a de-multiplexer.
- $CDC_{in} = x'_1 x'_2 x'_3 x'_4 + x_1 x_2 + x_1 x_3 + x_1 x_4 + x_2 x_3 + x_2 x_4 + x_3 x_4$.
- Outputs observed when $\begin{bmatrix} x_1 \\ x_4 \end{bmatrix} = \mathbf{1}$

$$ODC_{out} = \begin{bmatrix} x'_1 \\ x'_1 \\ x'_4 \\ x'_4 \end{bmatrix}$$

Example


overall external *don't care* **set**

© GDM

$$\mathbf{DC}_{ext} = \mathbf{CDC}_{in} + \mathbf{ODC}_{out} = \begin{bmatrix} x'_1 + x_2 + x_3 + x_4 \\ x'_1 + x_2 + x_3 + x_4 \\ x'_4 + x_2 + x_3 + x_1 \\ x'_4 + x_2 + x_3 + x_1 \end{bmatrix}$$

Internal *don't care* conditions

© GDM

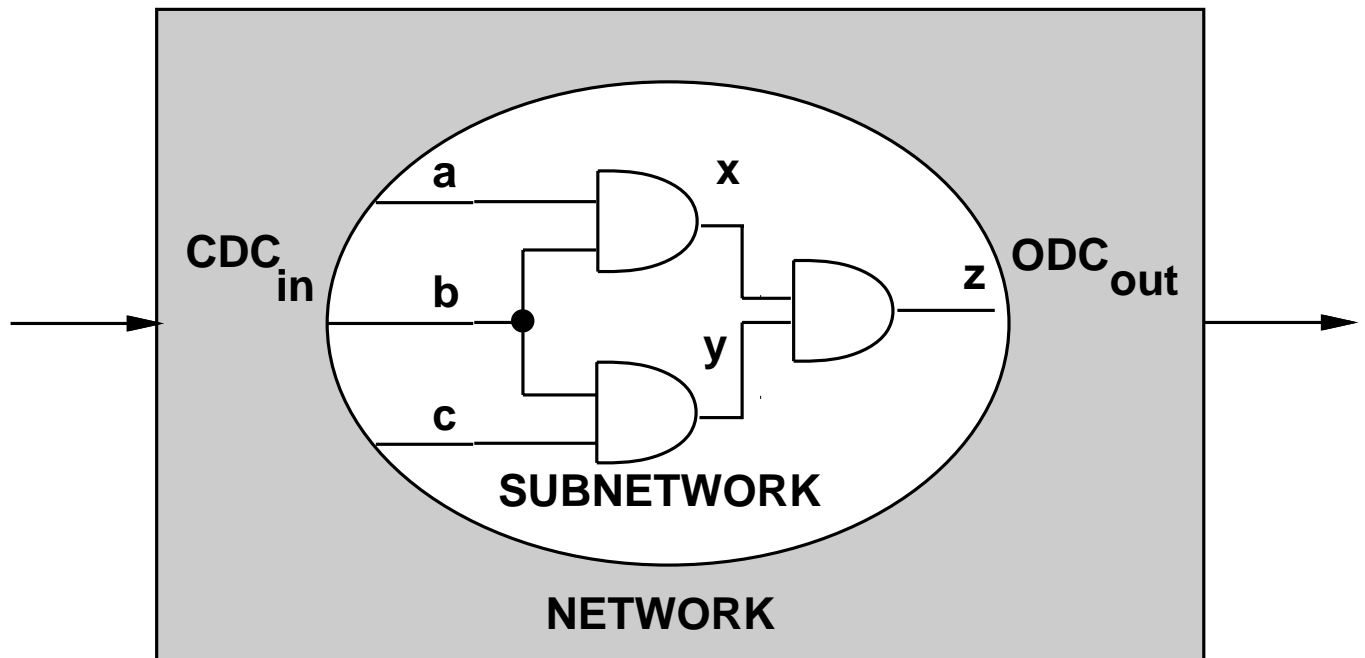


Internal *don't care* conditions

© GDM

- Induced by the network structure.
- *Controllability don't care* conditions:
 - Patterns never produced at the inputs of a subnetwork.
- *Observability don't care* conditions:
 - Patterns such that the outputs of a subnetwork are not observed.

Example

© GDM

 

- CDC of v_y includes $ab'x + a'x'$.
- Minimize f_y to obtain: $\widetilde{f}_y = ax + a'c$.

Satisfiability *don't care* conditions

© GDM

- Invariant of the network:

$$- x = f_x \rightarrow x \neq f_x \subseteq SDC.$$

- $$SDC = \sum_{v_x \in V^G} x \oplus f_x$$

- Useful to compute controllability *don't cares* .

CDC computation

© GDM

- Network traversal algorithm:
 - Consider different *cuts* moving from input to output.
- Initial CDC is CDC_{in} .
- Move *cut* forward.
 - Consider SDC contributions of predecessors.
 - Remove unneeded variables by *consensus*.


CDC computation

© GDM


```
CONTROLLABILITY( $G_n(V, E)$  ,  $CDC_{in}$ ) {  
     $C = V^I$ ;  
     $CDC_{cut} = CDC_{in}$ ;  
    foreach vertex  $v_x \in V$  in topological order {  
         $C = C \cup v_x$ ;  
         $CDC_{cut} = CDC_{cut} + f_x \oplus x$ ;  
         $D = \{v \in C \text{ s.t. all dir. succ. of } v \text{ are in } C\}$   
        foreach vertex  $v_y \in D$   
             $CDC_{cut} = \mathcal{C}_y(CDC_{cut})$ ;  
         $C = C - D$ ;  
    };  
     $CDC_{out} = CDC_{cut}$ ;  
}
```

Example


© GDM

 

(a)

 

(b)

 

(c)

Example

© GDM

- Assume $CDC_{in} = x'_1 x'_4$.
- Select vertex v_a :
 - Contribution to CDC_{cut} : $a \oplus (x_2 \oplus x_3)$.
 - Drop variables $D = \{x_2, x_3\}$ by consensus:
 - $CDC_{cut} = x'_1 x'_4$.
- Select vertex v_b :
 - Contribution to CDC_{cut} : $b \oplus (x_1 + a)$.
 - * $CDC_{cut} = x'_1 x'_4 + b \oplus (x_1 + a)$.
 - Drop variable x_1 by consensus:
 - * $CDC_{cut} = b' x'_4 + b' a$.
- ...
- $CDC_{out} = e' = z'_2$.

CDC computation by image computation


© GDM

- Network behavior at *cut*: \mathbf{f} .
- CDC_{cut} is just the complement of the *image* of $(CDC_{in})'$ with respect to \mathbf{f} .
- CDC_{cut} is just the complement of the *range* of \mathbf{f} when $CDC_{in} = \emptyset$.
- Range can be computed recursively.
 - Terminal case: scalar function.
 - * Range of $y = f(\mathbf{x})$ is $y + y'$ (any value) unless f (or f') is a tautology and the range is y (or y').


Example

© GDM

RANGE VECTORS

 

0 0 1

 


0 1 1


- $range(\mathbf{f}) = d \ range((b + c)|_{d=bc=1}) + d' \ range((b + c)|_{d=bc=0})$
- When $d = 1$, then $bc = 1 \rightarrow b + c = 1$ is TAUTOLOGY.
- If I choose 1 as top entry in output vector:
 - the bottom entry is also 1.
 - $\begin{bmatrix} 1 \\ ? \end{bmatrix} \rightarrow \begin{bmatrix} 1 \\ 1 \end{bmatrix}$
- When $d = 0$, then $bc = 0 \rightarrow b + c = \{0, 1\}$.
- If I choose 0 as top entry in output vector:
 - the bottom entry can be 0 or 1.
- $range(\mathbf{f}) = de + d'(e + e') = de + d' = d' + e$

Example


© GDM

 

(a)

 

(b)

 


(c)

$$\mathbf{f} = \begin{bmatrix} f^1 \\ f^2 \end{bmatrix} = \begin{bmatrix} (x_1 + a)(x_4 + a) \\ (x_1 + a) + (x_4 + a) \end{bmatrix} = \begin{bmatrix} x_1 x_4 + a \\ x_1 + x_4 + a \end{bmatrix}$$

Example

© GDM

 

$$\begin{aligned}
 range(\mathbf{f}) &= \\
 &= d \ range(f^2|_{(x_1x_4+a)=1}) + \\
 &\quad d' \ range(f^2|_{(x_1x_4+a)=0}) \\
 &= d \ range(x_1 + x_4 + a|_{(x_1x_4+a)=1}) + \\
 &\quad d' \ range(x_1 + x_4 + a|_{(x_1x_4+a)=0}) \\
 &= d \ range(1) + d' \ range(a'(x_1 \oplus x_4)) \\
 &= de + d'(e + e') \\
 &= e + d'
 \end{aligned}$$

- $CDC_{out} = (e + d')' = de' = z_1 z_2'$.


Perturbation method

© GDM


- Modify network by adding an extra input δ .
- Extra input can flip polarity of a signal x .
- Replace local function f_x by $f_x \oplus \delta$.
- Perturbed terminal behavior: $\mathbf{f}^x(\delta)$.

Example


© GDM

 

(a)

 

(b)

 

(c)

Observability *don't care* conditions

© GDM

- Conditions under which a change in polarity of a signal x is not perceived at the outputs.
- Complement of the Boolean difference:
 - $\partial f / \partial x = f|_{x=1} \oplus f|_{x=0}$.
- Equivalence of perturbed function: $\mathbf{f}^x(0) \overline{\oplus} \mathbf{f}^x(1)$.

Observability *don't care* computation

© GDM

- Problem:
 - Outputs are not expressed as function of all variables.
 - If network is flattened to obtain **f**, it may explode in size.
- Requirement:
 - Local rules for ODC computation.
 - Network traversal.

Single-output network with tree structure

© GDM

- Traverse network tree.

- At root:

- ODC_{out} is given.


- At internal vertices:

- $ODC_x = (\partial f_y / \partial x)' + ODC_y$

 Example

© GDM


$$\begin{aligned}e &= b + c \\b &= x_1 + a_1 \\c &= x_4 + a_2\end{aligned}$$



- Assume $ODC_{out} = ODC_e = 0$.
- $ODC_b = (\partial f_e / \partial b)' = (b + c)|_{b=1} \bar{\oplus} (b + c)|_{b=0} = c$.
- $ODC_c = (\partial f_e / \partial c)' = b$.
- $ODC_{x_1} = ODC_b + (\partial f_b / \partial x_1)' = c + a_1$.
- ...

General networks


© GDM

 

- Fanout reconvergence.
- For each vertex with two (or more) fanout stems:
 - The contribution of the ODC along the stems cannot be added *tout court*.
 - Interplay of different paths.
- More elaborate analysis.

Two-way fanout stem

© GDM

 

- Compute ODC sets associated with edges.
- Combine ODCs at vertex.
- Formula derivation:
 - Assume two equal perturbations on the edges.
 - $\mathbf{ODC}_x = \mathbf{f}^{x_1, x_2}(1, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 0)$

ODC formula derivation

© GDM

$$\begin{aligned}\mathbf{ODC}_x &= \mathbf{f}^{x_1, x_2}(1, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 0) \\ &= \mathbf{f}^{x_1, x_2}(1, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 0) \\ &\quad \oplus (\mathbf{f}^{x_1, x_2}(0, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 1)) \\ &= (\mathbf{f}^{x_1, x_2}(1, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 1)) \\ &\quad \oplus (\mathbf{f}^{x_1, x_2}(0, 1) \oplus \mathbf{f}^{x_1, x_2}(0, 0)) \\ &= \mathbf{ODC}_{x, y} \big|_{\delta_2=1} \oplus \mathbf{ODC}_{x, z} \big|_{\delta_1=0} \\ &= \mathbf{ODC}_{x, y} \big|_{x_2=x'} \oplus \mathbf{ODC}_{x, z} \big|_{x_1=x} \\ &= \mathbf{ODC}_{x, y} \big|_{x=x'} \oplus \mathbf{ODC}_{x, z}\end{aligned}$$

- Because $x = x_1 = x_2$.

Multi-way stems Theorem

 © GDM

- Let $v_x \in V$ be any internal or input vertex.
- Let $\{x_i, i = 1, 2, \dots, p\}$ be the edge vars corresponding to $\{(x, y_i) ; i = 1, 2, \dots, p\}$.
- Let \mathbf{ODC}_{x, y_i} , $i = 1, 2, \dots, p$ the edge ODCs.
- $\mathbf{ODC}_x = \overline{\bigoplus}_{i=1}^p \mathbf{ODC}_{x, y_i} |_{x_{i+1}=\dots=x_p} = x'$

Observability *don't care* algorithm

© GDM


```

OBSERVABILITY( $G_n(V, E)$  ,  $\mathbf{ODC}_{out}$ ) {
  foreach vertex  $v_x \in V$  in reverse topological order {
    for ( $i = 1$  to  $p$ )
       $\mathbf{ODC}_{x,y_i} = (\partial f_{y_i} / \partial x)' \mathbf{1} + \mathbf{ODC}_{y_i}$ ;
       $\mathbf{ODC}_x = \bigoplus_{i=1}^p \mathbf{ODC}_{x,y_i} |_{x_{i+1}=\dots=x_p = x'}$ ;
    }
  }
}


```

Example

© GDM

 

(a)

 

(b)

$$\mathbf{ODC}_d = \begin{pmatrix} 0 \\ 1 \end{pmatrix} ; \mathbf{ODC}_e = \begin{pmatrix} 1 \\ 0 \end{pmatrix} ; \mathbf{ODC}_c = \begin{pmatrix} b' \\ b \end{pmatrix} ; \mathbf{ODC}_b = \begin{pmatrix} c' \\ c \end{pmatrix}$$

$$\mathbf{ODC}_{a,b} = \begin{pmatrix} c' + x_1 \\ c + x_1 \end{pmatrix} = \begin{pmatrix} a'x'_4 + x_1 \\ a + x_4 + x_1 \end{pmatrix}$$

$$\mathbf{ODC}_{a,c} = \begin{pmatrix} b' + x_4 \\ b + x_4 \end{pmatrix} = \begin{pmatrix} a'x'_1 + x_4 \\ a + x_1 + x_4 \end{pmatrix}$$

$$\begin{aligned} \mathbf{ODC}_a &= \mathbf{ODC}_{a,b|a=a'} \bar{\oplus} \mathbf{ODC}_{a,c} = \begin{pmatrix} ax'_4 + x_1 \\ a' + x_4 + x_1 \end{pmatrix} \bar{\oplus} \begin{pmatrix} a'x'_1 + x_4 \\ a + x_1 + x_4 \end{pmatrix} = \\ &= \begin{pmatrix} x_1x_4 \\ x_1 + x_4 \end{pmatrix} \end{aligned}$$

Transformations with *don't cares*

© GDM

- Boolean simplification:
 - Use standard minimizer (Espresso).
 - Minimize the number of literals.
- Boolean substitution:
 - Simplify a function by adding an extra input.
 - Equivalent to simplification with global *don't care* conditions.

Example

Boolean substitution

© GDM

- Substitute $q = a + cd$ into $f_h = a + bcd + e$ to get $f_h = a + bq + e$.
- SDC set: $q \oplus (a + cd) = q'a + q'cd + qa'(cd)'$.
- Simplify $f_h = a + bcd + e$ with $q'a + q'cd + qa'(cd)'$ as *don't care*.
- Simplification yields $f_h = a + bq + e$.
- One literal less by changing the support of f_h .

Single-vertex optimization

© GDM

```
SIMPLIFY_SV(  $G_n(V, E)$  ){  
  repeat {  
     $v_x$  = selected vertex ;  
    Compute the local don't care set  $DC_x$ ;  
    Optimize the function  $f_x$  ;  
  }until (no more reduction is possible)  
}
```

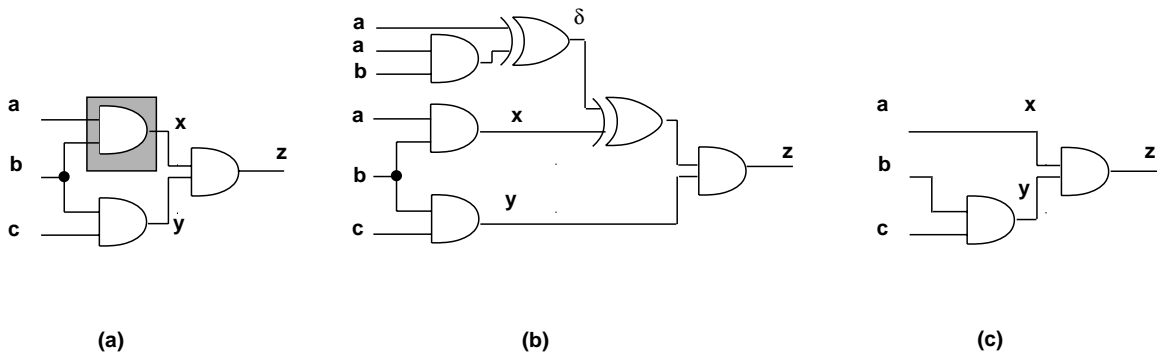

Optimization and perturbations

© GDM

- Replace f_x by g_x .
- Perturbation $\delta_x = f_x \oplus g_x$.
- Condition for feasible replacement:
 - Perturbation bounded by local *don't care* set
 - $\delta_x \subseteq \mathbf{DC}_{ext} + \mathbf{ODC}_x$
 - If x not a primary input consider also CDC set.

Example

© GDM



- No external *don't care* set.
- Replace AND by wire: $g_x = a$
- Analysis:
 - $\delta = f_x \oplus g_x = ab \oplus a = ab'$.
 - $ODC_x = y' = b' + c'$.
 - $\delta = ab' \subseteq DC_x = b' + c' \Rightarrow$ feasible!

Degrees of freedom

© GDM

- Fully represented by *don't care* conditions:
 - External *don't cares* .
 - Internal observability and controllability.
- *Don't cares* represent an *upper bound* on the perturbation.
- Approximations:
 - Use smaller *don't care* sets to speed-up the computation.





Multiple-vertex optimization

© GDM

- Simplify more than one local function at a time.
- Potentially better (more general) approach.
- Analysis:
 - Multiple perturbations.
- Condition for feasible replacement:
 - *Upper and lower bounds* on the perturbation.
 - Boolean relation model.

Example

© GDM

    


- The two perturbations are related.
- Cannot change simultaneously:
 - $ab \rightarrow a$.
 - $cb \rightarrow c$.

Multiple-vertex optimization

Boolean relation model

© GDM

 

| <i>a</i> | <i>b</i> | <i>c</i> | <i>x, y</i> |
|----------|----------|----------|----------------|
| 0 | 0 | 0 | { 00, 01, 10 } |
| 0 | 0 | 1 | { 00, 01, 10 } |
| 0 | 1 | 0 | { 00, 01, 10 } |
| 0 | 1 | 1 | { 00, 01, 10 } |
| 1 | 0 | 0 | { 00, 01, 10 } |
| 1 | 0 | 1 | { 00, 01, 10 } |
| 1 | 1 | 0 | { 00, 01, 10 } |
| 1 | 1 | 1 | { 11 } |

Multiple-vertex optimization

Boolean relation model

© GDM

- Compute Boolean relation:
 - Flatten the network. Analyze patterns.
 - Derive equivalence relation from ODCs.
- Use relation minimizer.

- Example of minimum function:

| a | b | c | x, y |
|-----|-----|-----|--------|
| 1 | * | * | 10 |
| * | 1 | 1 | 01 |

Multiple-vertex optimization Boolean relation model

© GDM

```
SIMPLIFY_MVR(  $G_n(V, E)$  ){  
  repeat {  
     $U$  = selected vertex subset;  
    foreach vertex  $v_x \in U$   
      Compute  $OCD_x$ ;  
      Determine the equiv. classes of the Boolean relation  
        of the subnetwork induced by  $U$ ;  
      Find an optimal function compatible with the relation  
        using a relation minimizer;  
    }until (no more reduction is possible);  
}
```


Multiple-vertex optimization compatible *don't cares*

© GDM

- Determine *compatible don't cares* :
 - CODCs: subset of ODCs.
 - Decouple dependencies.
 - Reduced degrees of freedom.
- Using compatible ODCs, only *upper bounds* on the perturbation need to be satisfied.


Example two perturbations

© GDM

- First vertex:
 - CODC equal to its ODC set.
 - $CODC_{x_1} = ODC_{x_1}$.
- The second vertex:
 - CODC smaller than its ODC to be safe enough to allow transformations permitted by the first ODC.
 - $CODC_{x_2} = \mathcal{C}_{x_1}(ODC_{x_2}) + ODC_{x_2}ODC'_{x_1}$
- Order dependence.

Example first vertex v_y


© GDM

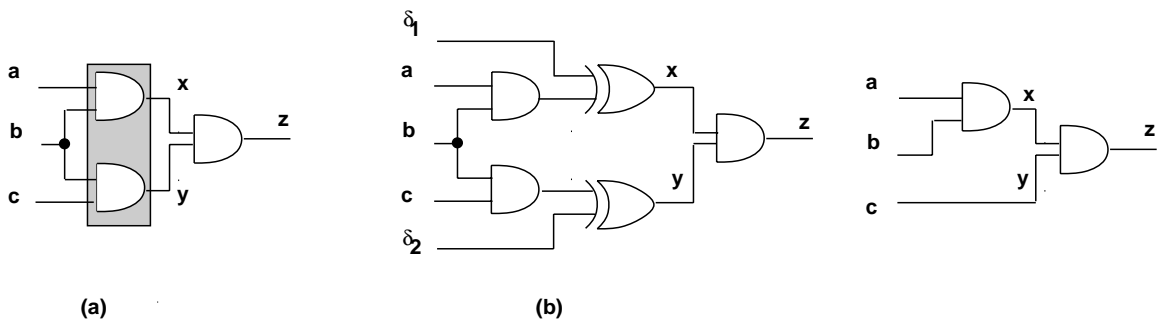

- $CODC_y = ODC_y = x' = b' + a'$
- $ODC_x = y' = b' + c'$
- $CODC_x = C_y(ODC_x) + ODC_x(ODC_y)' = C_y(y') + y'x = y'x = (b' + c')ab = abc'$.

Example (2)

© GDM

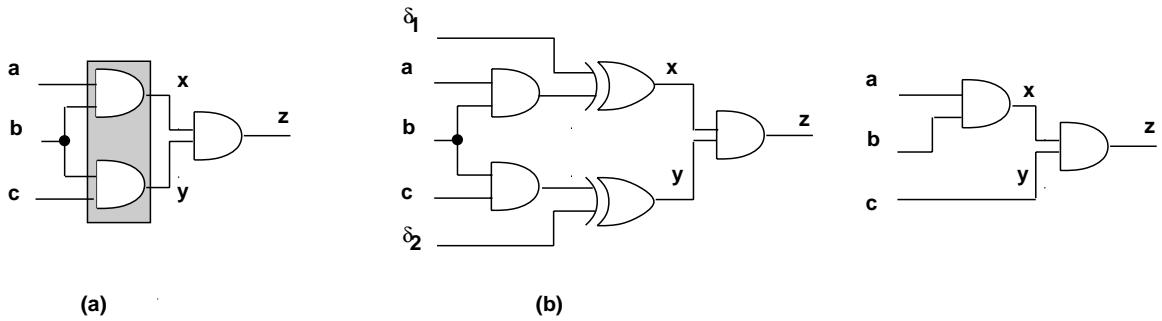

- Allowed perturbation:

- $f_y = bc \rightarrow g_y = c.$

- $\delta_y = bc \oplus c = b'c \subseteq CODC_y = b' + a'.$

- Disallowed perturbation:

- $f_x = ab \rightarrow g_x = a.$

- $\delta_x = ab \oplus a = ab' \not\subseteq CODC_x = abc'.$

- The converse holds if v_x is the first vertex.

Multiple-vertex optimization compatible *don't cares*

© GDM

```
SIMPLIFY_MV(  $G_n(V, E)$  ){  
  repeat {  
     $U$  = selected vertex subset;  
    foreach vertex  $v_x \in U$   
      Compute  $COC D_x$  and the corresponding  
      local don't care subset  $\widetilde{DC}_x$ ;  
      Optimize simultaneously the functions at  $U$ ;  
  }until (no more reduction is possible);  
}
```

Summary

Boolean methods

© GDM

- Boolean methods exploit *don't care* sets and simplification of logic representations.
- *Don't care* set computation:
 - Controllability and observability.
- Single and multiple transformations.

Synthesis and testability

© GDM

- Testability:
 - Ease of testing a circuit.
- Assumptions:
 - Combinational circuit.
 - Single or multiple *stuck-at* faults.
- Full testability:
 - Possible to generate test set for all faults.
 - Restrictive interpretation.

Test for *stuck-ats*

© GDM

- Net y stuck-at 0.
 - Input pattern that sets y to true.
 - Observe output.
 - Output of faulty circuit differs.
- Net y stuck-at 1.
 - Same, but set y to false.
- Need *controllability* and *observability*.

Test sets

don't care interpretation

© GDM

- Stuck-at 0 on net y .
 - $\{\mathbf{t} | y(\mathbf{t}) \cdot ODC'_y(\mathbf{t}) = 1\}$.
- Stuck-at 1 on net y .
 - $\{\mathbf{t} | y'(\mathbf{t}) \cdot ODC'_y(\mathbf{t}) = 1\}$.




Using testing methods for synthesis

© GDM

- Redundancy removal.
 - Use TPG to search for untestable faults.
- If stuck-at 0 on net y is untestable:
 - Set $y = 0$.
 - Propagate constant.
- If stuck-at 1 on y is untestable:
 - Set $y = 1$.
 - Propagate constant.

Example

© GDM

 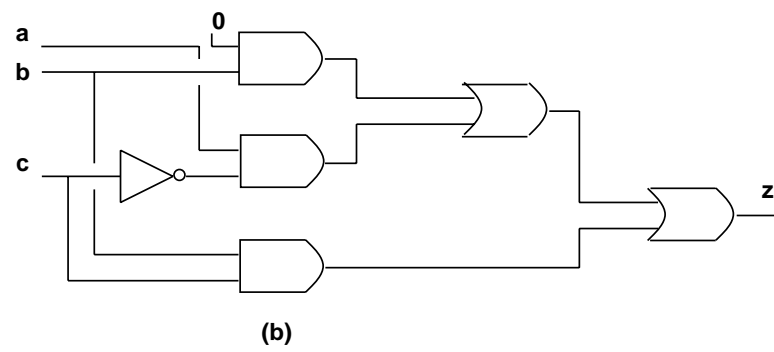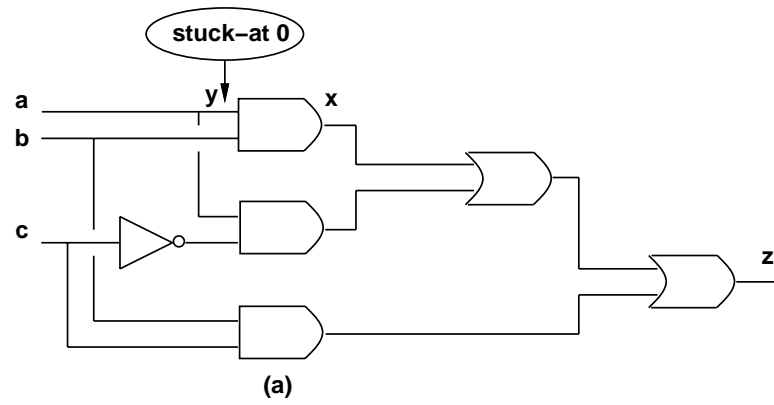

Redundancy removal and perturbation analysis

© GDM



- Stuck-at 0 on y .
 - y set to 0. Namely $g_x = f_x|_{y=0}$.
 - Perturbation:
 - * $\delta = f_x \oplus f_x|_{y=0} = y \cdot \partial f_x / \partial y$.
- Perturbation is feasible \Leftrightarrow fault is untestable.
 - No input vector \mathbf{t} can make $y(\mathbf{t}) \cdot ODC'_y(\mathbf{t})$ true.
 - No input vector can make $y(\mathbf{t}) \cdot ODC'_x(\mathbf{t}) \cdot \partial f_x / \partial y$ true.
 - * because $ODC_y = ODC_x + (\partial f_x / \partial y)'$.

Redundancy removal and perturbation analysis

© GDM

- Assume untestable stuck-at 0 fault.
- $y \cdot ODC'_x \cdot \partial f_x / \partial y \subseteq SDC$.
- Local *don't care* set:
 - $DC_x \supseteq ODC_x + y \cdot ODC'_x \cdot \partial f_x / \partial y$.
 - $DC_x \supseteq ODC_x + y \cdot \partial f_x / \partial y$.
- Perturbation $\delta = y \cdot \partial f_x / \partial y$.
 - Included in the local *don't care* set.

Synthesis for testability

© GDM

- Synthesize networks that are fully testable.
 - Single stuck-at faults.
 - Multiple stuck-at faults.
- Two-level forms.
- Multiple-level networks.

Two-level forms


© GDM

- Full testability for single stuck-at faults:
 - Prime and irredundant cover.
- Full testability for multiple stuck-at faults:
 - Prime and irredundant cover when:
 - * Single-output function.
 - * No product term sharing.
 - * Each component is PI.

Example

$$f = a'b' + b'c + ac + ab$$

© GDM

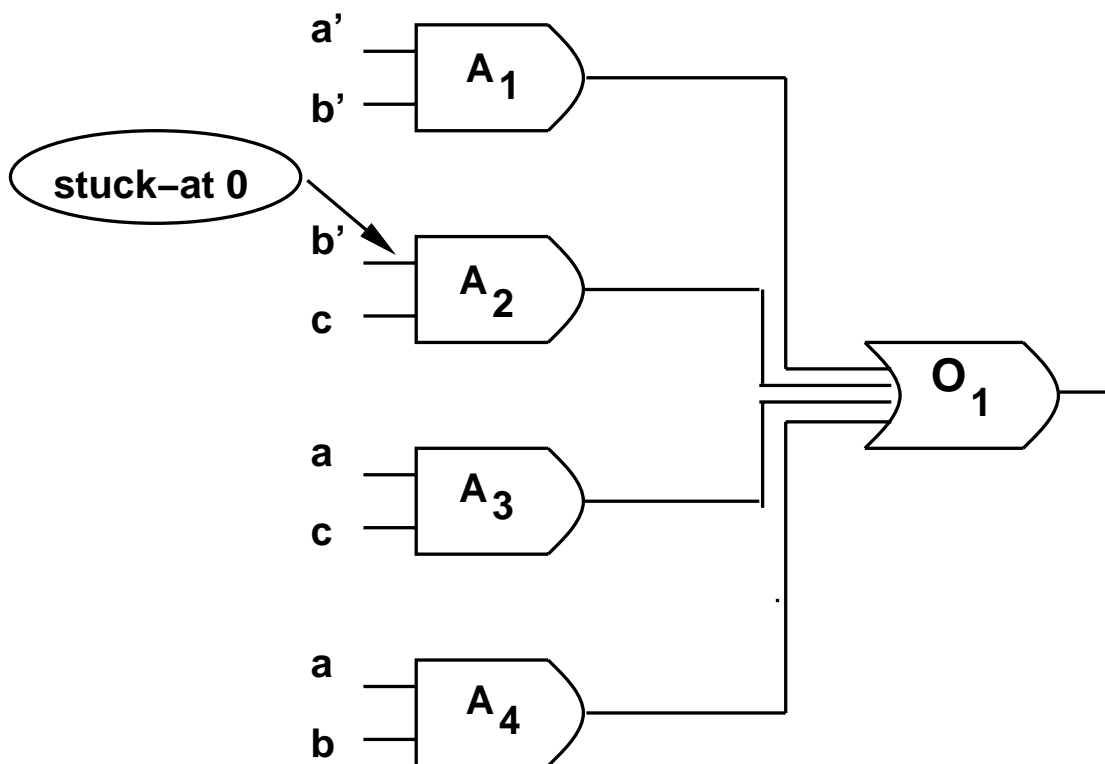

Multiple-level networks

Definitions

© GDM

- A logic network $G_n(V, E)$,
with local functions in *sum of product* form.
- Prime and irredundant (PI):
 - No literal nor implicant of any local function can be dropped.
- Simultaneously prime and irredundant (SPI):
 - No subset of literals and/or implicants can be dropped.

Multiple-level networks

Theorems

© GDM

- A logic network is PI and only if:
 - its AND-OR implementation is fully testable for single stuck-at faults.
- A logic network is SPI if and only if:
 - its AND-OR implementation is fully testable for multiple stuck-at faults.

Multiple-level networks Synthesis

© GDM

- Compute full local *don't care* sets.
 - Make all local functions PI w.r. to *don't care* sets.
- Pitfall:
 - *Don't cares* change as functions change.
- Solution:
 - Iteration (Espresso-MLD).
- If iteration converges, network is fully testable.

Multiple-level networks Synthesis

© GDM

- Flatten to two-level form.
 - When possible – no size explosion.
- Make SPI by disjoint logic minimization.
- Reconstruct multiple-level network:
 - *Algebraic transformations preserve multifault testability.*

Summary

© GDM

- Synergy between synthesis and testing.
- Testable networks correlate to small-area networks.
- *Don't care* conditions play a major role.